

Lab 2 Extra

IN3170 - Microelectronics

Andreas Engøy, Erik Røset & Daniel Tran

May 2024

Contents

1 Task 1	1
1.1 Objective	1
1.2 Theory	1
1.3 Equipment	2
1.4 Method	2
1.5 Results	4
1.6 Discussion	5

1 Task 1

1.1 Objective

The objective of this task is to build two CMOS inverter chains of different length and probing before the first and after the last inverter. The purpose of this is to measure and calculate the propagation delay a single inverter without knowing the added capacitance of the scope probe or directly measuring the delay of just one inverter.

1.2 Theory

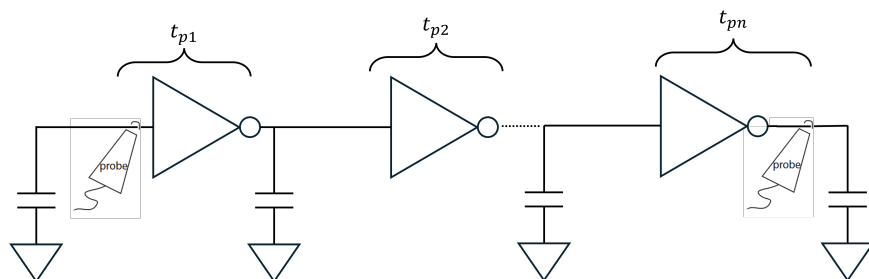


Figure 1: Illustration of the different propagation delays for a inverter chain.

The total propagation delay of a chain of inverters is the sum of the propagation delay of each inverter. The oscilloscope probes used to measure the input and output signals add capacitance to the circuit, which can affect the measurement of the propagation delay. By measuring at the start and end of a inverter chain the added delay from the parasitic capacitance of the probes can be

merged with the propagation delay of the first and last inverter as shown in figure 1. I.e. the total propagation delay of a chain of inverters can be written as:

$$t_{p.tot} = t_{p1} + t_{p2} + \dots + t_{pn} \quad (1)$$

Where t_{p1} and t_{pn} also include the propagation delay introduced by the probes.

By then measuring the propagation delay of a chain of inverters with n inverters and subtracting the propagation delay of a chain of inverters with $n - 1$ inverters, the difference between the two would be the propagation delay of a single inverter without the added delay from the probes. This can be written as:

$$t_{1inv} = t_{p.tot(n)} - t_{p.tot(n-1)} \quad (2)$$

1.3 Equipment

Component	Model	Quantity
Hex Schmitt-Trigger Inverters	SN74HC1	1
Oscilloscope	HP54622	1
Waveform generator	HP33120	1
Voltage source	HPE3631	1
Breadboard	~	1

Table 1: List of components used in task 1.

1.4 Method

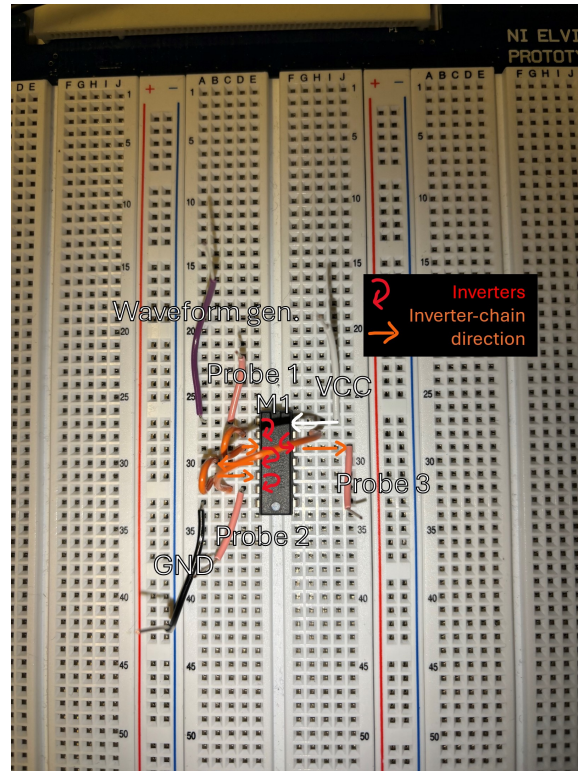


Figure 2: Picture of the setup for task 1.

On a breadboard, using $M1$ (SN74HC1) we built two inverter chains, one with 3 inverters and one with 4 inverters. At pin 1 a square wave with a frequency of 400 Hz, V_{pp} of 2.1 V and V_{off} of 1.1 V was connected. At pin 14 a 5 V power supply was connected. Pin 7 was connected to ground.

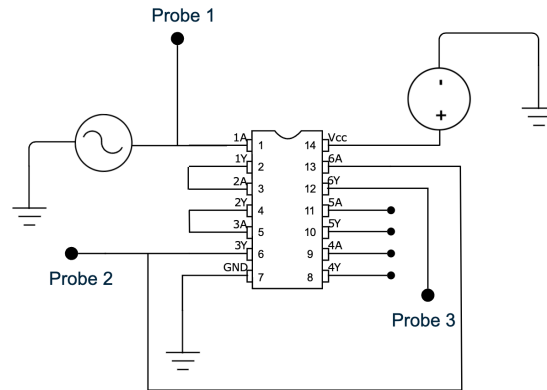


Figure 3: Schematic of the setup for task 1.

In figure 2 and 3; probe 1 is used to measure the input signal, probe 2 is used to measure the output after the third inverter and probe 3 is used to measure the output after the fourth inverter.

On the oscilloscope, channel 1 is connected to probe 1 and channel 2 is connected to probe 2 and 3, depending on if measuring for three or four inverters respectively. To reduce noise on the output, the built-in averaging filter of the oscilloscope was used. The X- and Y-axis were scaled to show one rising/falling edge of the input and output.

1.5 Results

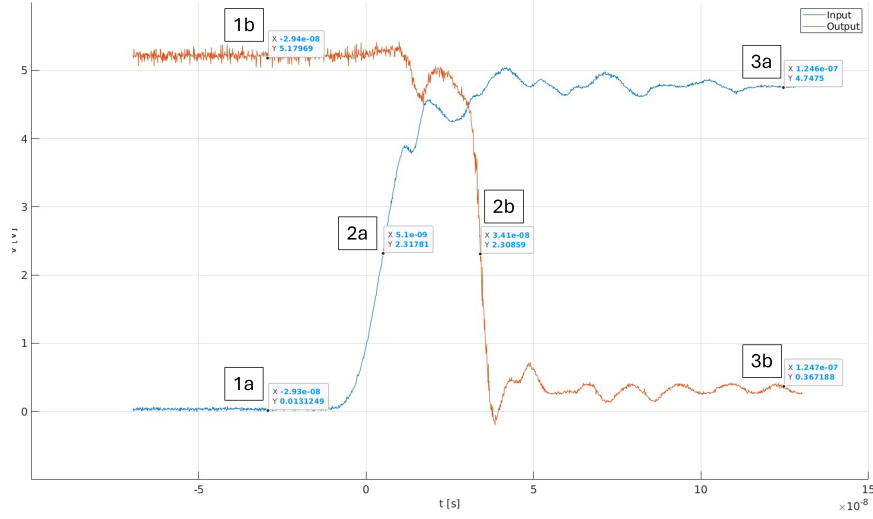


Figure 4: Rising edge of the input and falling edge of the output for the three inverter chain, with labeled marked points on the plot.

In figure 4 point 2a is used as the switching point for the input signal, somewhere around 50 % of the rising edge. This point is estimated using point 1a as the low-signal and point 3a as the high-signal of the input signal. The same is done for the output signal in figure 4 using the points marked with 'b' instead.

The total propagation delay for the three inverter-chain is calculated as follows:

$$t_{in} = 5.1e-9 \text{ s} \quad (3)$$

$$t_{out} = 3.41e-8 \text{ s} \quad (4)$$

$$t_{3inv} = t_{out} - t_{in} = 2.9e-8 \text{ s} \quad (5)$$

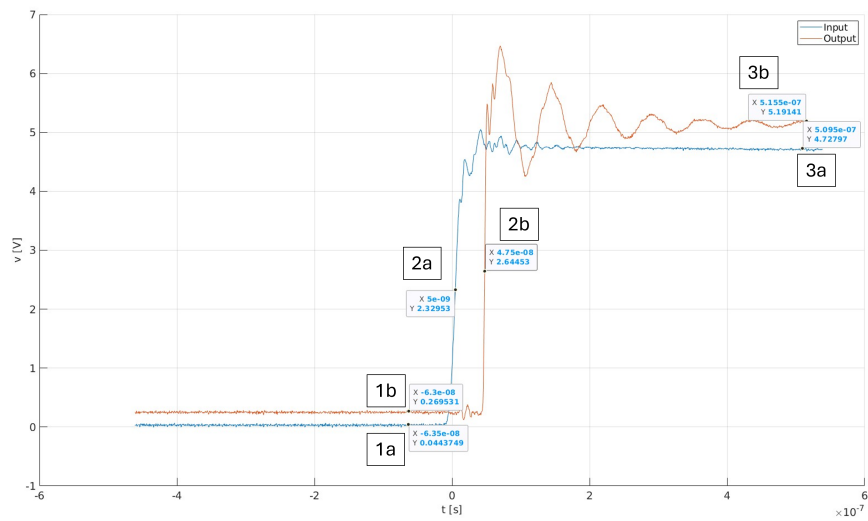


Figure 5: Rising edges of the input and output for the four inverter chain, with labeled marked points on the plot.

The same method for finding the total propagation delay is used for the four inverter-chain in figure 5 and is as follows:

$$t_{in} = 5\text{e-}9 \text{ s} \quad (6)$$

$$t_{out} = 4.75\text{e-}8 \text{ s} \quad (7)$$

$$t_{4inv} = t_{out} - t_{in} = 4.45\text{e-}8 \text{ s} \quad (8)$$

The values found in equation 5 and 8 are then used in equation 2 to calculate the propagation delay of a single inverter as follows:

$$t_{1inv} = t_{4inv} - t_{3inv} = 1.55\text{e-}8 \text{ s} \quad (9)$$

1.6 Discussion

In the results section, both inverter chains are only plotted for either rising or falling edge. This is done on the assumption of equal time for both edges. This is not necessarily true, but the difference is assumed to be negligible.

The calculation of the switching points in figure 4 and 5 have some inaccuracies. The high and low signal points '1' and '3' are not exact. From the figures it is highly likely that the inverters are a underdampened system given that the measurements at probe 2 and 3 have a period of oscillating before stabilising at transition. To measure more accurately, the high points are set a bit further from the edges, giving the signal time to settle. This does not necessarily give a fully accurate measurement, but it is more likely to give a more stable one.

As mentioned, the switching points were calculated to be the halfway between points 1 and 3 in figure 4 and 5. The points marked 2a and 2b are not necessarily the exact switching points, as the oscilloscope resolution limits how exact the measurements could be.

As mentioned, an averaging filter was used to reduce noise on the output signal. It is still important to mention that the assignment was not done fully controlled. There is highly likely several stochastic variables tempering with the measurements.